


Electrical Systems

Tim McLain

Brigham Young University


Basic elements

- Resistor

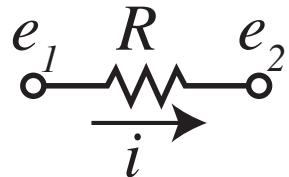

$$e_1 - e_2 = Ri$$


- Capacitor

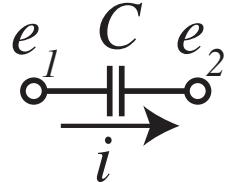

$$e_1 - e_2 = \frac{1}{C} \int i dt$$

$$i = C \frac{de_c}{dt} = C \frac{d}{dt} (e_1 - e_2) = Cs(e_1 - e_2)$$

- Inductor

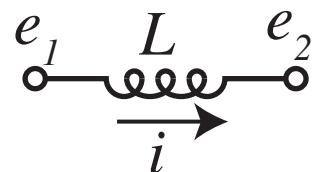

$$e_1 - e_2 = L \frac{di}{dt}$$

$$si = \frac{di}{dt} = \frac{1}{L} (e_1 - e_2)$$


Resistors in series or parallel

- Resistors in series add



$$R_T = R_1 + R_2 + R_3$$

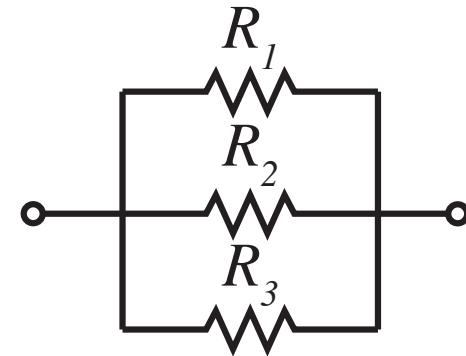- Resistors in parallel add by reciprocals



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Capacitors and inductors in series or parallel

- Capacitors in series add like resistors in parallel (reciprocals)

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

- Capacitors in parallel add

$$C_T = C_1 + C_2 + C_3$$

- Inductors in series add


$$L_T = L_1 + L_2 + L_3$$

- Inductors in parallel add like resistors in parallel (reciprocals)

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Kirchoff's current law (KCL)

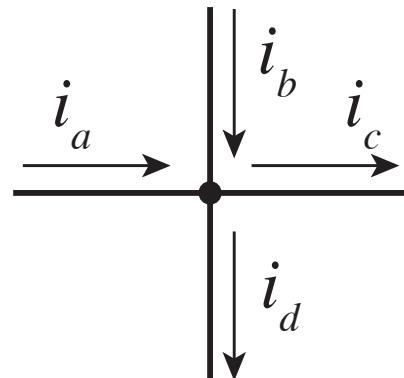- Node: A point of connection between two or more circuit components
- KCL: The sum of all currents at a node is equal to zero




$$\text{KCL} \rightarrow i_a + i_b - i_c - i_d = 0$$

Deriving equations of “motion”


1. Draw a schematic of the circuit. Identify each component with a unique symbolic value. It is usually helpful to give each component a unique number.
2. Identify the nodes of the circuit and assign each one a letter to identify it.
3. For each component, assign the direction of positive current flow and indicate it on the circuit diagram. The current in the n^{th} component will be known as i_n .
4. Write an equation for the current in each component using the established physical relation for each type of component.
5. Define state variables to be *capacitor voltages* and *inductor currents*. Write component equations for capacitors and inductors in state-variable form.
6. Write node equations using KCL for each node that is not directly connected to a voltage source. Where possible, express node voltages in terms of capacitor and input voltages.
7. Use the remaining component equations and node equations to reduce the differential equations so that they contain only the state variables and inputs.

Example 1

1. Draw a schematic of the circuit. Identify each component with a unique symbolic value. It is usually helpful to give each component a unique number.
2. Identify the nodes of the circuit and assign each one a letter to identify it.
3. For each component, assign the direction of positive current flow and indicate it on the circuit diagram. The current in the n^{th} component will be known as i_n .
4. Write an equation for the current in each component using the established physical relation for each type of component.
5. Define state variables to be *capacitor voltages* and *inductor currents*. Write component equations for capacitors and inductors in state-variable form.
6. Write node equations using KCL for each node that is not directly connected to a voltage source. Where possible, express node voltages in terms of capacitor and input voltages.
7. Use the remaining component equations and node equations to reduce the differential equations so that they contain only the state variables and inputs.

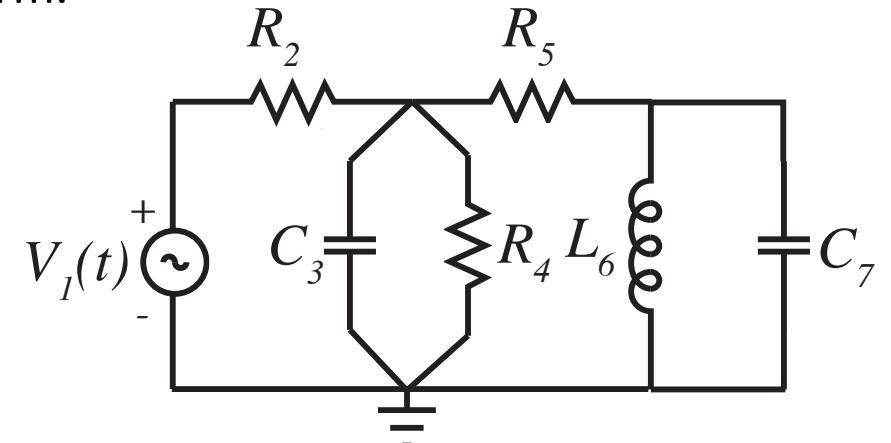

Example 1

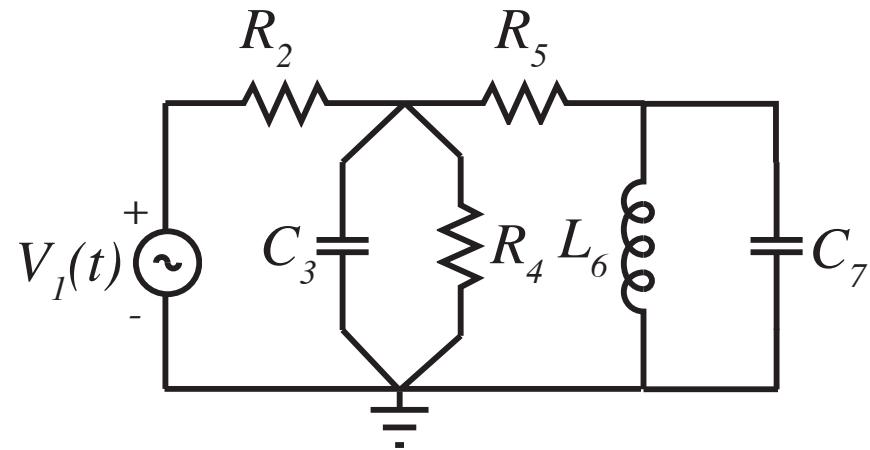


$$se_3 = \frac{1}{C_3} \left[\frac{V_1(t)}{R_2} - \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right) e_3 + \frac{1}{R_5} e_7 \right]$$


$$se_7 = \frac{1}{C_7} \left[\frac{e_3}{R_5} - \frac{e_7}{R_5} - i_6 \right]$$

$$si_6 = \frac{e_7}{L_6}$$


Example 2

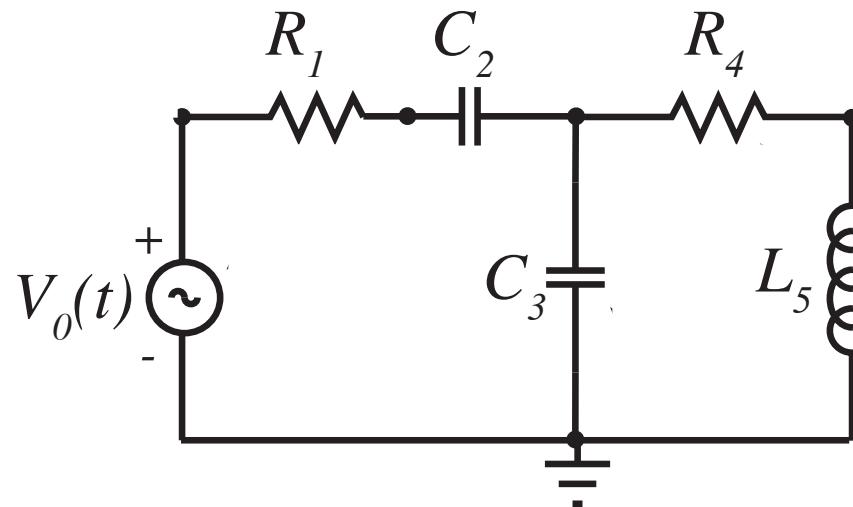

Example 6.2.13

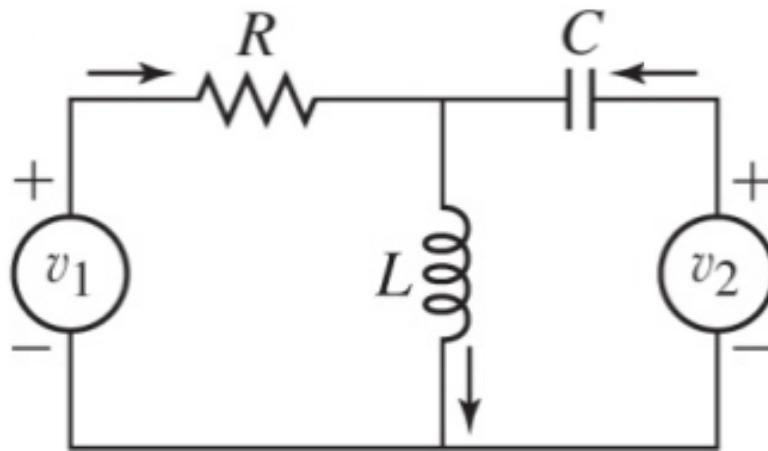


Example 3

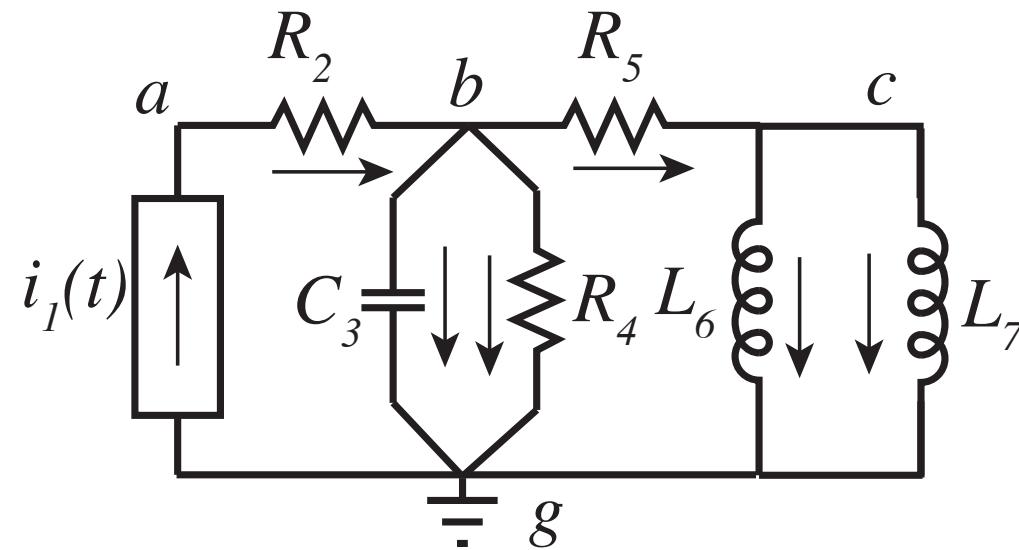

Example 3 – Energy storage elements that are not independent

Example 3

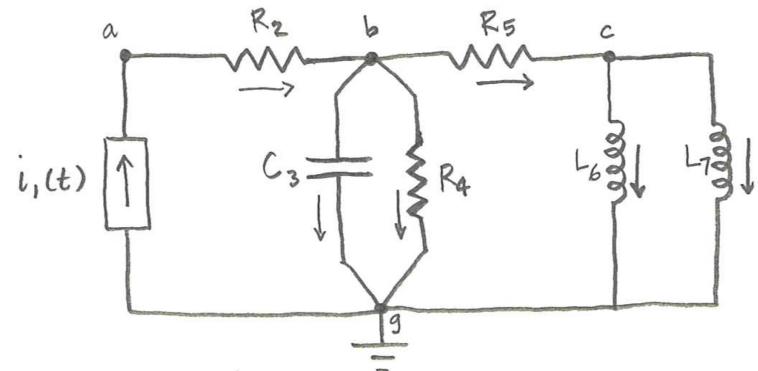

Node Equations:

$$\textcircled{a} \quad i_1 = i_2$$

$$\textcircled{b} \quad i_2 = i_3 + i_4 + i_5$$

$$\textcircled{c} \quad i_5 = i_6 + i_7$$

State Variables: e_3, i_6, i_7

Inputs: $i_1(t)$

Component Relations:

$$i_2 = \frac{e_a - e_b}{R_2} \quad i_4 = \frac{e_b}{R_4} \quad i_5 = \frac{e_b - e_c}{R_5}$$

$$i_3 = C_3 s e_3 \quad i_6 = \frac{1}{sL_6} e_c \quad i_7 = \frac{1}{sL_7} e_c$$

$$e_3 = e_b$$

Example 3

State Variable Equations:

$$se_3 = \frac{1}{C_3} i_3 = \frac{1}{C_3} (i_2 - i_4 - i_5) = \frac{1}{C_3} (i_1(t) - \frac{e_b}{R_4} - i_6 - i_7)$$


$$\underline{se_3 = \frac{1}{C_3} \left[i_1(t) - \frac{e_3}{R_4} - (i_6 + i_7) \right]}$$

$$si_6 = \frac{1}{L_6} e_c$$

$$\underline{si_6 = \frac{1}{L_6} [e_3 - R_5(i_6 + i_7)]}$$

$$si_7 = \frac{1}{L_7} e_c$$
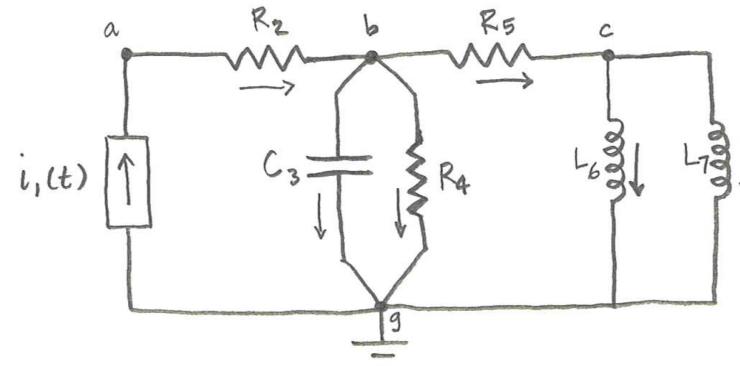
$$\underline{si_7 = \frac{1}{L_7} [e_3 - R_5(i_6 + i_7)]}$$



Note: L_6 and L_7 are not independent!

$$i_6 = \frac{e_c}{s} L_6 \quad i_7 = \frac{e_c}{s} L_7 \quad \Rightarrow \frac{e_c}{s} = \frac{i_7}{L_7}$$

$$i_6 = \frac{L_6}{L_7} i_7 \quad \text{state variables related by an algebraic expression rather than an ODE.}$$

Only 2 states required to represent this system!


Example 3

$$* i_6 + i_7 = \frac{L_6}{L_7} i_7 + i_7 = \left(\frac{L_6}{L_7} + 1 \right) i_7$$

State equations can be simplified to :

$$se_3 = \frac{1}{C_3} \left[i_1(t) - \frac{e_3}{R_4} - \left(\frac{L_6}{L_7} + 1 \right) i_7 \right]$$

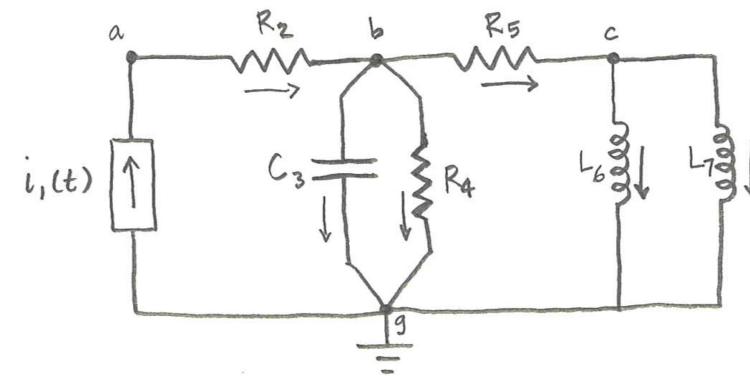
$$si_7 = \frac{1}{L_7} \left[e_3 - R_5 \left(\frac{L_6}{L_7} + 1 \right) i_7 \right]$$



- * Simplified equations could have also been obtained by recognizing that L_6 and L_7 are in parallel and by replacing them with a single inductance :

$$\boxed{L_{eq} = \frac{L_6 L_7}{L_6 + L_7}}$$

Example 4 – Coupled resistances

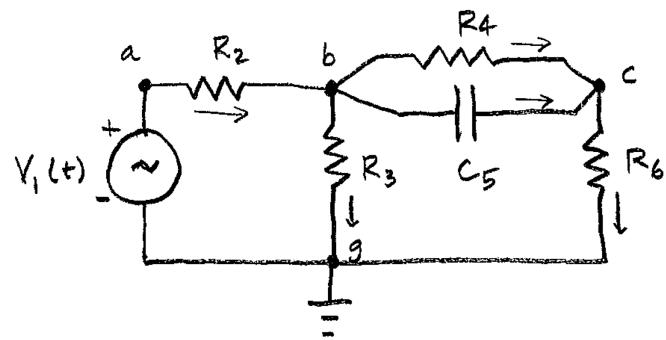

State Variables : e_5

Node Eqns :

$$\textcircled{b} \quad i_2 = i_3 + i_4 + i_5$$

$$\textcircled{c} \quad i_4 + i_5 = i_6$$

Component Relations

$$i_2 = \frac{V_1(t) - e_b}{R_2}$$


$$i_3 = \frac{e_b}{R_3}$$

$$i_4 = \frac{e_b - e_c}{R_4}$$

$$i_6 = \frac{e_c}{R_6}$$

$$i_5 = C_5 s e_5, \quad e_5 = e_b - e_c \quad \Rightarrow \quad e_c = e_b - e_5$$

Example 4 – Coupled resistances

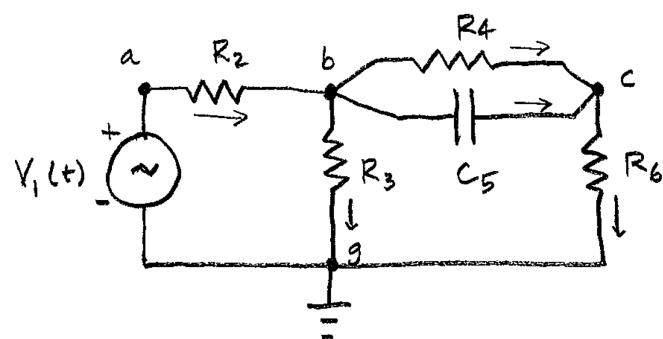

Component Relations

$$i_2 = \frac{V_1(t) - e_b}{R_2} \quad i_3 = \frac{e_b}{R_3} \quad i_4 = \frac{e_b - e_c}{R_4} \quad i_6 = \frac{e_c}{R_6}$$

$$i_5 = C_5 \dot{e}_5, \quad e_5 = e_b - e_c \quad \Rightarrow \quad e_c = e_b - e_5$$

EOM:

$$\begin{aligned}\dot{e}_5 &= \frac{1}{C_5} i_5 \\ &= \frac{1}{C_5} [i_2 - i_3 - i_4] \\ &= \frac{1}{C_5} \left[\frac{V_1(t) - e_b}{R_2} - \frac{e_b}{R_3} - \frac{e_5}{R_4} \right]\end{aligned}$$

$$e_b = ? \quad \text{want in terms of } e_5, V_1(t)$$

use 2nd node equation


$$i_4 + i_5 = i_6$$

$$\frac{e_5}{R_4} + C_5 \dot{e}_5 = \frac{e_c}{R_6} = \frac{e_b - e_5}{R_6}$$

$$\Rightarrow e_b = R_6 \left[\frac{e_5}{R_4} + \frac{e_5}{R_6} + C_5 \dot{e}_5 \right]$$

Example 4 – Coupled resistances

Substituting

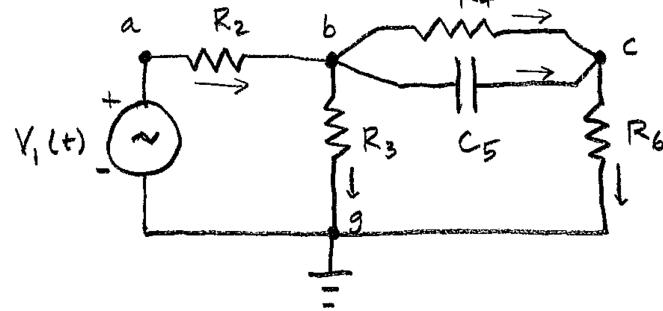

$$c_5 \dot{e}_5 = \frac{V_1(t)}{R_2} - \left(\frac{R_6}{R_2} + \frac{R_6}{R_3} \right) \left[\frac{e_5}{R_4} + \frac{e_5}{R_6} + c_5 \dot{e}_5 \right] - \frac{e_5}{R_4}$$

$\xrightarrow{\quad R_6 \frac{(R_2 + R_3)}{R_2 R_3} \quad}$

Solve for \dot{e}_5 :

$$\left[1 + \frac{R_6(R_2 + R_3)}{R_2 R_3} \right] c_5 \dot{e}_5 = \frac{V_1(t)}{R_2} - \frac{R_6(R_2 + R_3)}{R_2 R_3} \left(\frac{e_5}{R_4} + \frac{e_5}{R_6} \right) - \frac{e_5}{R_4}$$

$$\dot{e}_5 = \frac{R_2 R_3}{R_2 R_3 + R_6(R_2 + R_3)} \left[\frac{V_1(t)}{R_2} - \frac{1}{R_4} \left(1 + \frac{(R_2 + R_3)(R_4 + R_6)}{R_2 R_3 R_4} \right) e_5 \right]$$

Some messy algebra, but nothing too hard ...