

Electrical Systems


Active Circuits

Tim McLain

Brigham Young University


Basic elements

- Resistor

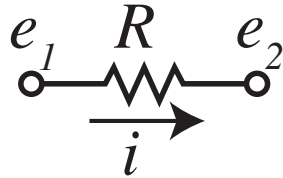

$$e_1 - e_2 = Ri$$


- Capacitor

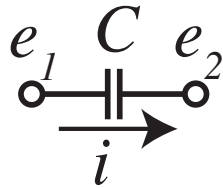

$$e_1 - e_2 = \frac{1}{C} \int i dt$$

$$i = C \frac{de_c}{dt} = C \frac{d}{dt}(e_1 - e_2) = Cs(e_1 - e_2)$$

- Inductor

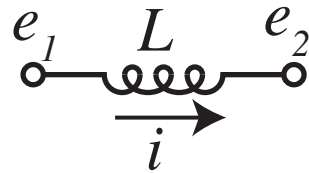


$$e_1 - e_2 = L \frac{di}{dt}$$

$$si = \frac{di}{dt} = \frac{1}{L}(e_1 - e_2)$$

Deriving equations of “motion”

1. Draw a schematic of the circuit. Identify each component with a unique symbolic value. It is usually helpful to give each component a unique number.
2. Identify the nodes of the circuit and assign each one a letter to identify it.
3. For each component, assign the direction of positive current flow and indicate it on the circuit diagram. The current in the n^{th} component will be known as i_n .
4. Write an equation for the current in each component using the established physical relation for each type of component.
5. Define state variables to be *capacitor voltages* and *inductor currents*. Write component equations for capacitors and inductors in state-variable form.
6. Write node equations using KCL for each node that is not directly connected to a voltage source. Where possible, express node voltages in terms of capacitor and input voltages.
7. Use the remaining component equations and node equations to reduce the differential equations so that they contain only the state variables and inputs.

Op-amps – The ideal model

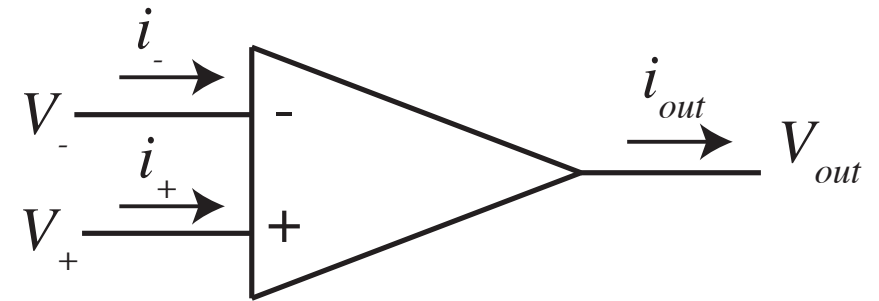

Three assumptions:

1. Both inputs have infinite impedance. The op-amp does not draw current from any input.

$$i_- = i_+ = 0$$

2. The op-amp has infinite gain. When feedback is used, the input voltages are equal.

$$V_+ = V_-$$

3. The op-amp has zero output impedance. Any devices that draw current from the output will have no effect on the output voltage value.

Example P6.29

